

# **Case Study Mechatronic System Simulation**

***Task-1: Block oriented and object-oriented simulation of a  
2nd order RC low pass filter***

## **Report by**

Prasad Raju Kalidindi – 12100544


Omar Shokr – 12101363

Mahadev Prem – 12100009

Tom Jojo Palamattam – 821354

## **Supervised by**

Prof. Dr.-Ing. Peter Firsching

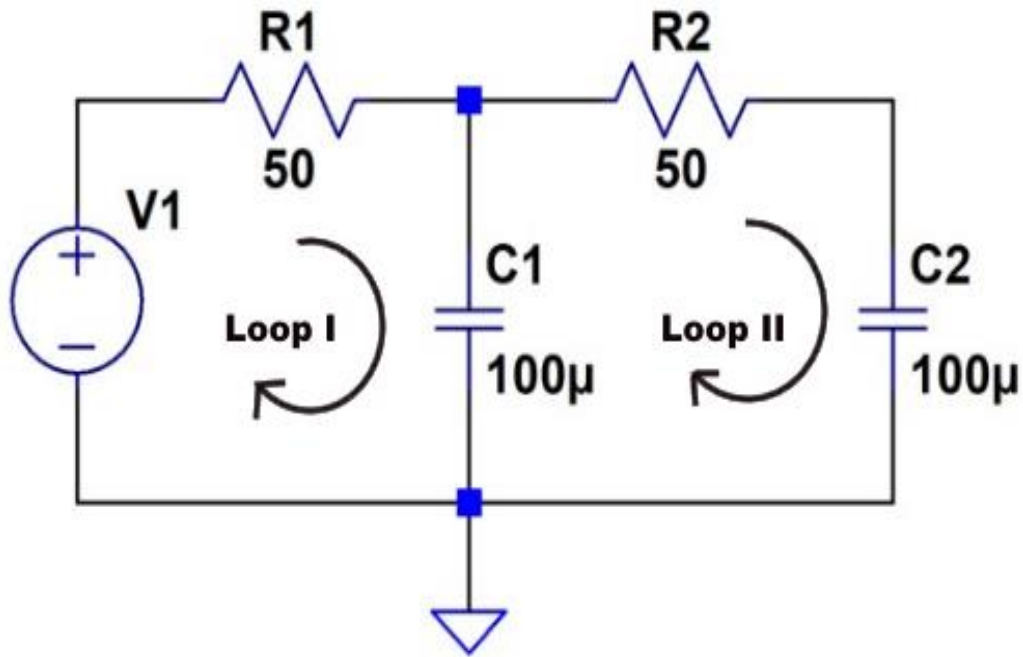

**Fig 1: 2<sup>nd</sup> Order RC Low Pass Filter**

**a) Determination of the Steady state equations**

Given state variables are  $U_{c_1}(t)$  and  $U_{c_2}(t)$

Lets assume

$$x_1 = U_{c_1}(t) \text{ and } x_2 = U_{c_2}(t)$$

And

$$I_1 = C_1 \dot{x}_1 \text{ and } I_2 = C_2 \dot{x}_2$$

Applying the Kirchoff's Voltage Law

**Loop I**

$$V_1 = (I_1 + I_2)R_1 + U_{c_1}(t)$$

$$V_1 = (C_1 \dot{x}_1 + C_2 \dot{x}_2)R_1 + x_1 \longrightarrow \text{ (i) }$$

**Loop II**

$$-x_1 + I_2 R_2 + x_2 = 0$$

$$-x_1 + C_2 \dot{x}_2 R_2 + x_2 = 0$$

$$C_2 \dot{x}_2 R_2 = x_1 - x_2$$

$$\Rightarrow \dot{x}_2 = \frac{1}{C_2 R_2} x_1 - \frac{1}{C_2 R_2} x_2 \longrightarrow \text{ (I) }$$

Substituting equation (I) in (i)

$$\begin{aligned}
 \Rightarrow V_1 &= C_1 R_1 \dot{x}_1 + C_2 \left[ \frac{x_1}{C_2 R_2} - \frac{x_2}{C_2 R_2} \right] R_1 + x_1 \\
 V_1 &= C_1 x_1^* R_1 + \frac{R_1}{R_2} x_1 - \frac{R_1}{R_2} x_2 + x_1 \\
 C_1 R_1 \dot{x}_1 &= -\frac{R_1}{R_2} x_1 + \frac{R_1}{R_2} x_2 - x_1 + V_1 \\
 \dot{x}_1 &= -\frac{1}{C_1 R_1} x_1 - \frac{x_1}{C_1 R_2} + \frac{1}{C_1 R_2} x_2 + \frac{V_1}{C_1 R_1} \\
 \dot{x}_1 &= \left[ -\frac{1}{C_1 R_2} - \frac{1}{C_1 R_2} \right] x_1 + \frac{1}{C_1 R_2} x_2 + \frac{V_1}{C_1 R_1} \longrightarrow \text{(II)}
 \end{aligned}$$

The state equations are:

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -\frac{1}{C_1 R_1} - \frac{1}{C_1 R_2} & \frac{1}{C_1 R_2} \\ \frac{1}{C_2 R_2} & -\frac{1}{C_2 R_2} \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} \frac{1}{C_1 R_1} \\ 0 \end{bmatrix} [V_1]$$

We have,

$$V_1 = 10V, R_1 = 50\Omega$$

$$C_1 = 100\mu F, R_2 = 50\Omega$$

$$C_2 = 100\mu F$$

Solving for  $a_{11}, a_{12}, a_{21}$  and  $a_{22}$

$$a_{11} = \frac{-1}{C_1 R_1} + \frac{-1}{C_2 R_2} = \frac{-1}{100 \times 50 \times 10^{-6}} + \frac{-1}{100 \times 50 \times 10^{-6}} \Rightarrow -400$$


$$a_{12} = \frac{1}{C_1 R_2} = \frac{1}{100 \times 50 \times 10^{-6}} \Rightarrow 200$$

$$a_{21} = \frac{1}{C_2 R_2} = \frac{1}{100 \times 50 \times 10^{-6}} \Rightarrow 200$$

$$a_{22} = -\frac{1}{C_2 R_2} = \frac{-1}{100 \times 50 \times 10^{-6}} \Rightarrow -200$$


$$b_1 = \frac{1}{C_1 R_1} = \frac{1}{100 \times 50 \times 10^{-6}} \Rightarrow 200$$

### b) Block Structure for Simulation in Scilab/Xcos

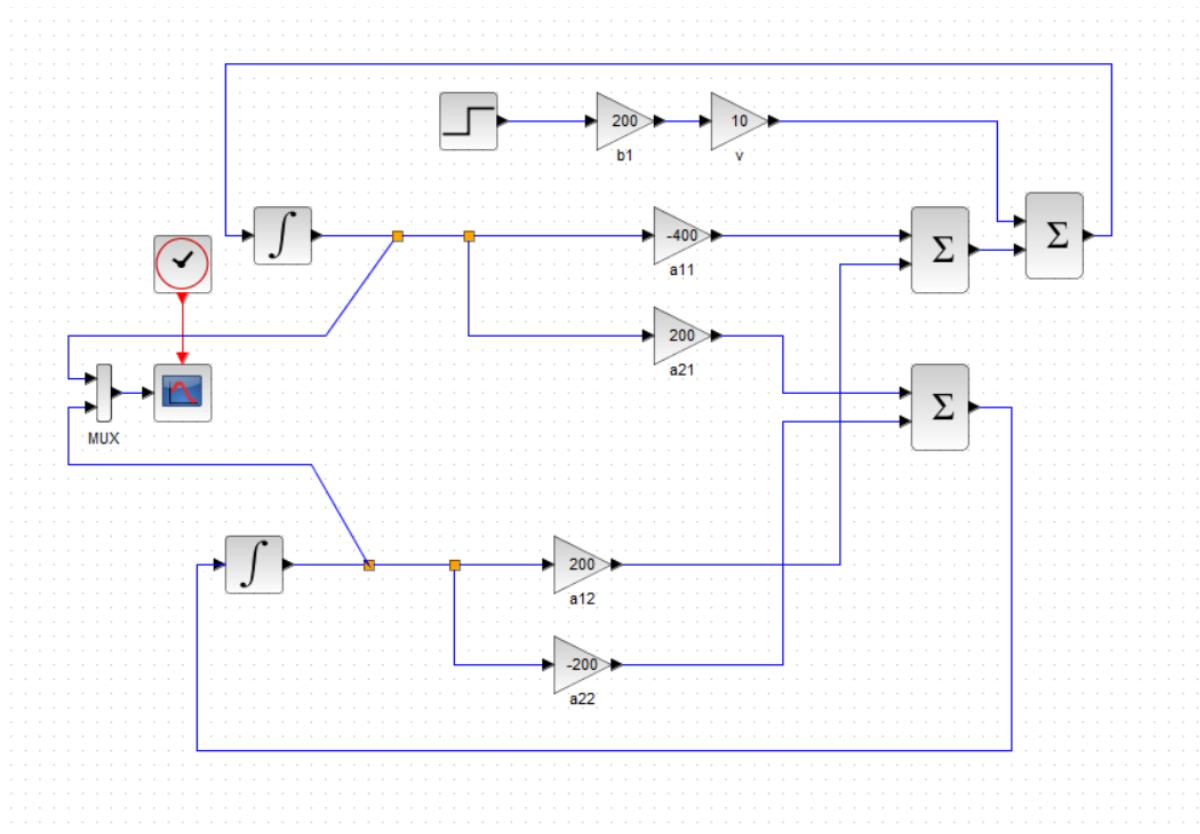

**Fig 2: Block diagram**

**c) Simulation in Scilab/Xcos the frequency response of UC1(t) of the filter**

```
report1.1 
1 R1=50;
2 R2=50;
3 C1=0.0001;
4 C2=0.0001;
5 a11=-1/(C1*R1)-1/(C1*R2);
6 a12=1/(C1*R2);
7 a21=1/(C2*R2);
8 a22=-1/(C2*R2);
9 b1=1/(C1*R1);
10 A=[a11 a12;a21 a22];
11 B=[b1;0];
12 F=syslin('c',A,B,[0 1]);
13 bode(F,1,100);
```

**Fig 3: Scilab Notes code for RC filter**

d) Circuit diagram of the RC filter with the help of LTspice

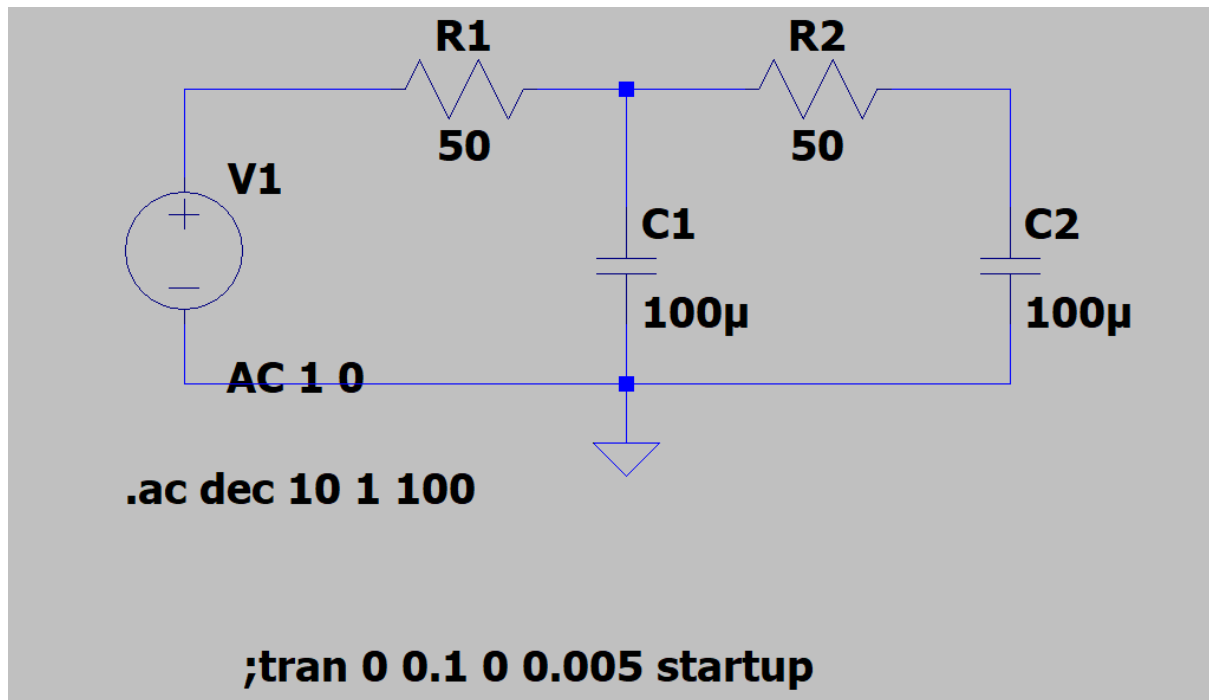


Fig 4: Circuit Diagram in LTspace

e) Comparing the results from Scilab and LTspace



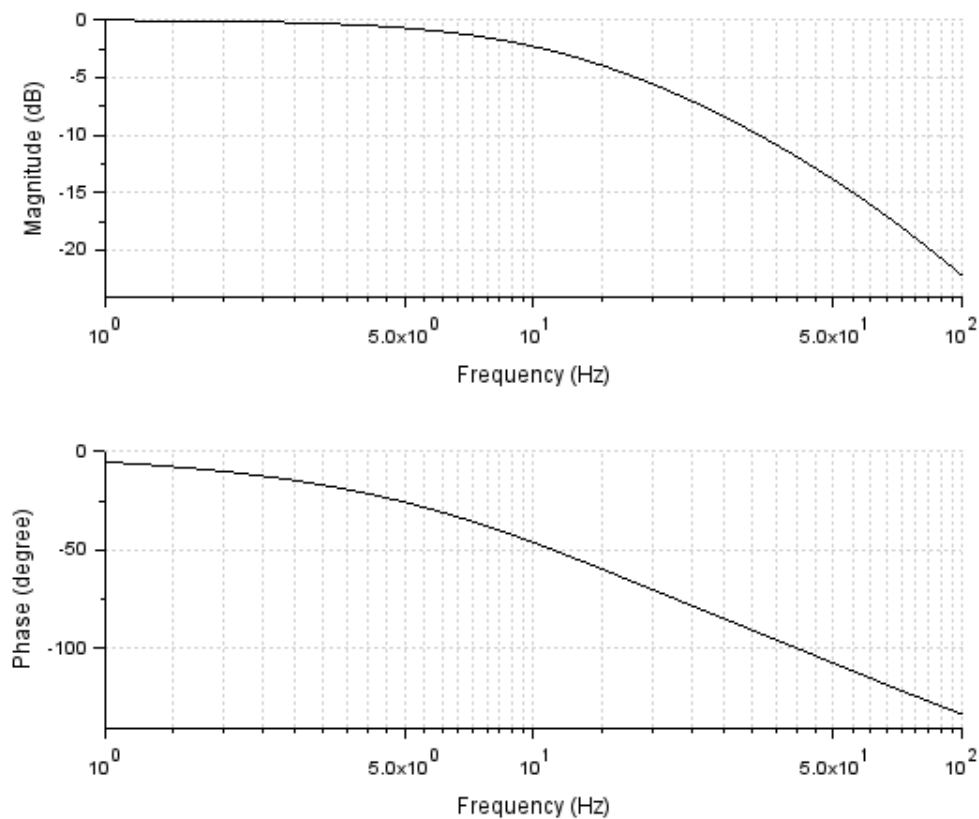


Fig 5: Bode plot of RC filter in Scilab

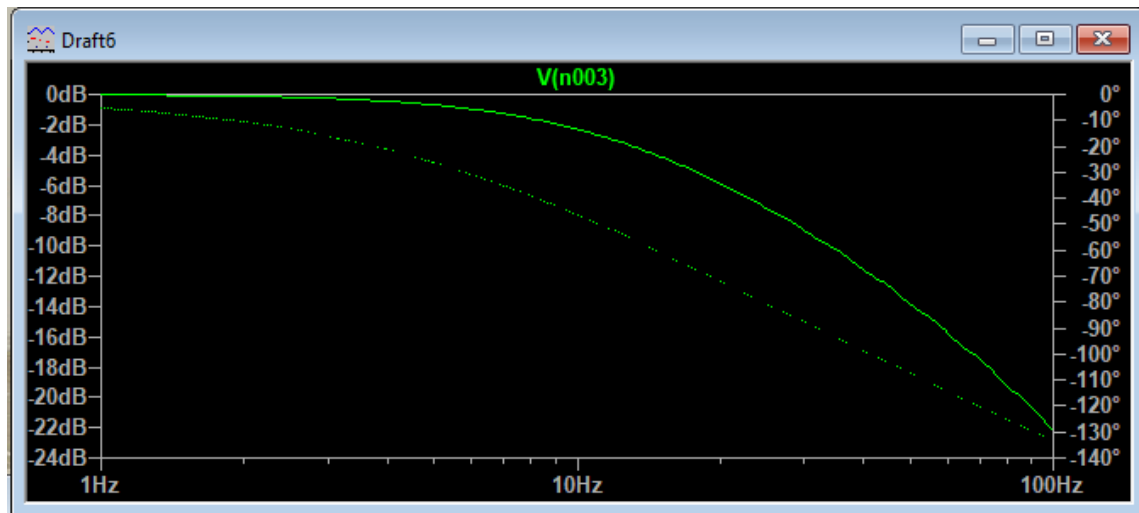

**Fig 6: AC Analysis Using LTspace**

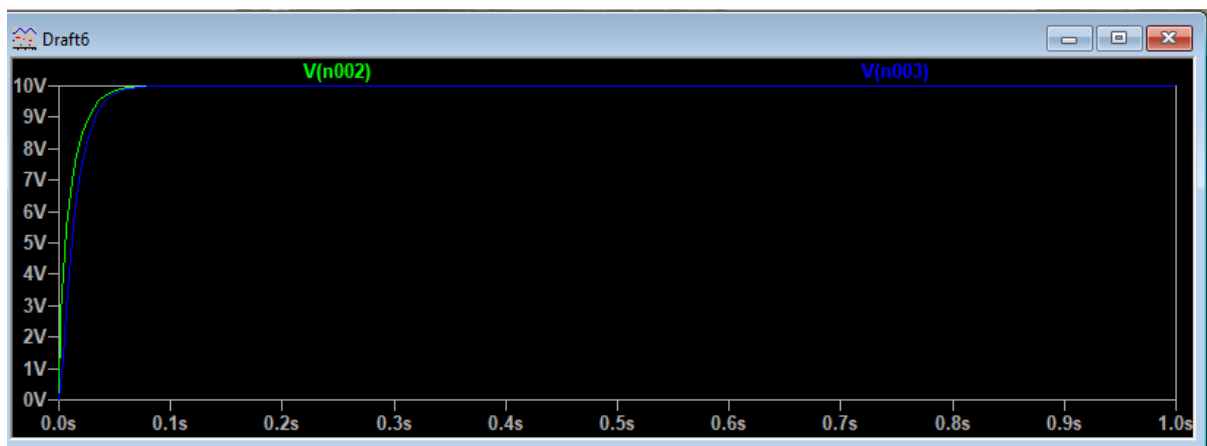

**Fig 7: Transient Analysis Using LTspace**

### COMMENTS:

- For block-oriented simulation, it describes the simulation steps including the mathematical calculations (summation, integration, differentiation. Etc) during the simulation itself. While object-oriented simulation describes the functional structure of the system only.
- In block-oriented simulation, there is fixed order of computation. While object-oriented simulation has variable order of computation.
- The re-usability of object-oriented simulation is depending on the components (R1, R2, C1, C2, V1), While re-usability in block-oriented simulation depends on very low level of mathematical operations.
- Block-oriented programming requires the derivation of state space equations and the calculation of coefficients whereas object-oriented programming does not require any calculations.
- Object-oriented method can be easily interpreted but block-oriented needs some time and skill.
- Any change in the circuit can be easily modified in object-oriented than in block-oriented.